 


Mod 6:

| Reset | Inc | Q2 | Q1 | Q0 | Q2+ | Q1+ | Q0+ |
|-------|-----|----|----|----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | X | X | X | X | 0 | 0 | 0 |



David DeGraw
 Lab #9: Stopwatch
 3/17/2015
 Q2+:

| | | Q2 Q1 | | | |
|----|---|-------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q0 | 0 | 0 | 0 | X | 1 |
| | 1 | 0 | 1 | X | 0 |

$$Q2+ = Q1 Q0 + Q2 Q0'$$

Q1+:

| | | Q2 Q1 | | | |
|----|---|-------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q0 | 0 | 0 | 1 | X | X |
| | 1 | 1 | 0 | X | 0 |

$$Q1+ = Q1 Q0' + Q2' Q1' Q0$$


Q0+:

| | | Q2 Q1 | | | |
|----|---|-------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q0 | 0 | 1 | 1 | 0 | 1 |
| | 1 | 0 | 0 | 0 | 0 |

$$Q0+ = Q2' Q0' + Q1' Q0'$$

Mod 10:

| Q3 | Q2 | Q1 | Q0 | Q3+ | Q2+ | Q1+ | Q0+ |
|----|----|----|----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |

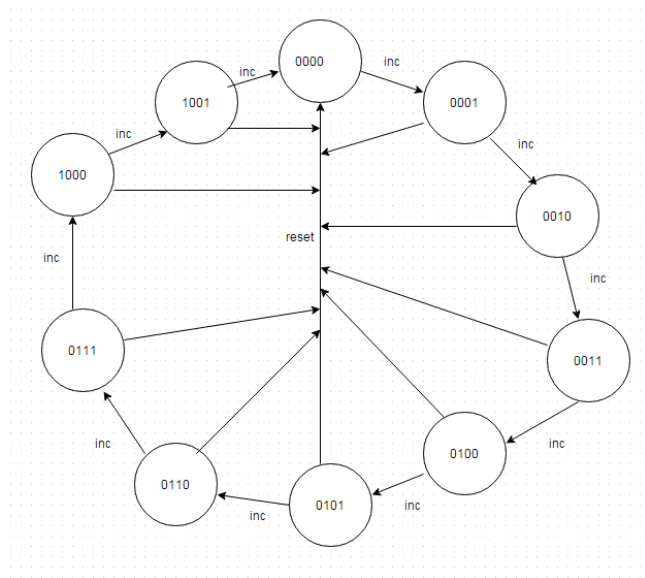

David DeGraw
 Lab #9: Stopwatch
 3/17/2015
 Q3+:

| | | AB | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| CD | 00 | 0 | 0 | X | 1 |
| | 01 | 0 | 0 | X | 0 |
| | 11 | 0 | 1 | X | 0 |
| | 10 | 0 | 0 | X | 0 |

$$Q3+ = Q2Q1Q0 + Q3Q1'Q0'$$

Q2+:

| | | AB | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| CD | 00 | 0 | 1 | X | 0 |
| | 01 | 0 | 1 | X | 0 |
| | 11 | 1 | 0 | X | 0 |
| | 10 | 0 | 1 | X | 0 |

$$Q2+ = Q2Q1' + Q2Q0' + Q3'Q2'Q1Q0$$

Q1+:

| | | AB | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| CD | 00 | 0 | 0 | X | 0 |
| | 01 | 1 | 1 | X | 0 |
| | 11 | 0 | 0 | X | 0 |
| | 10 | 1 | 1 | X | 0 |

$$Q1+ = Q3'Q1'Q0 + Q3'Q1Q0'$$

Q0+:

| | | AB | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| CD | 00 | 1 | 1 | X | 1 |
| | 01 | 0 | 0 | X | 0 |
| | 11 | 0 | 0 | X | 0 |
| | 10 | 1 | 1 | X | 1 |

$$Q0+ = Q0'$$

SR Latch:

```
module srLatch (set, reset, q);
  input set, reset;
  output q;

  wire w1, w2;

  nor(w1, set, q);
  nor(q, reset, w1);
endmodule
```

```
isim force add set 0 -time 0 -value 1 -time 20ns
isim force add reset 1 -time 0 -value 0 -time 10ns -value 1 -
time 30ns
```



David DeGraw
Lab #9: Stopwatch
3/17/2015
Mod 6:


```
module mod6counter(q, clken, inc, clk, reset);
    input clk, reset, inc;
    output reg [2:0] q;
    output clken;

    always @(posedge clk)
    begin
        if (reset)
            q <= 3'b000;
        else if (inc)
            q <= q + 3'b001;

        if (q == 3'b101 && inc)
            q <= 3'b000;
        end

        assign clken = (q == 3'b101 && inc) ? 1'b1 : 1'b0;
    endmodule

 isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add inc 1
isim force add reset 1 -time 0 -value 0 -time 20ns
```



David DeGraw
Lab #9: Stopwatch
3/17/2015

Mod 10:


```
module mod10counter(q, clken, inc, clk, reset);
    input clk, reset, inc;
    output reg [3:0] q;
    output clken;

    always @(posedge clk)
    begin
        if (reset)
            q <= 4'b0000;
        else if (inc)
            q <= q + 4'b0001;

        if (q == 4'b1001 && inc)
            q <= 4'b0000;
        end

        assign clken = (q == 4'b1001 && inc) ? 1'b1 : 1'b0;
    endmodule

 isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add inc 1
isim force add reset 1 -time 0 -value 0 -time 20ns
```



David DeGraw
Lab #9: Stopwatch
3/17/2015

Counter Block:

```


module counterBlock (d1, d2, d3, d4, inc, clk, reset);
    input inc, clk, reset;
    wire r1, r2, r3;
    wire [2:0] d2tmp;
    output [3:0] d1, d2, d3, d4;

    mod10counter thousandth (d4, r1, inc, clk, reset);
    mod10counter tenth (d3, r2, r1, clk, reset);
    mod6counter second (d2tmp, r3, r2, clk, reset);
    mod10counter minute (d1, clken, r3, clk, reset);

    assign d2 = {1'b0, d2tmp};
endmodule

isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add inc 1
isim force add reset 1 -time 0 -value 0 -time 20ns

```

 

David DeGraw
Lab #9: Stopwatch
3/17/2015

Test Bench:

```
module testBench (clk, reset, stop, sett, w3, seg, odp, w1);
    input clk, reset, sett, stop;
    wire [3:0] d1, d2, d3, d4;
    output [3:0] w3;
    wire srTemp, zero, tp;
    wire r1, r2, r3;
    wire [2:0] d2tmp;
    output odp;
    output [6:0] seg;
    output [1:0] w1;

    counterBlock c1 (d1, d2, d3, d4, zero, clk, reset);

    prog_timer t1 (clk, reset, srTemp, 24'd5000000, counter, zero, tp);

    srLatch sr (sett, stop, srTemp);

    controller47 seg7 (4'b1010, w3, d1, d2, d3, d4, seg, odp, clk, 0, w1);
endmodule

## clock pin for Nexys 2 Board
NET clk LOC = "B8"; # Bank = 0, Pin

## Buttons
NET reset LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch
#NET increment LOC = "D18"; # Bank = 1, Pin name = IP/VREF_1, Type :
NET stop LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch :
NET sett LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch :

## 7 segment display
NET seg[6] LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O
NET seg[5] LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O
NET seg[4] LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type :
NET seg[3] LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type
NET seg[2] LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O
NET seg[1] LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
NET seg[0] LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O
NET odp LOC = "C17"; # Bank = 1, Pin name = IO_L24N_1/LDC2, Typ

NET w3[0] LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type = I/O
NET w3[1] LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0, Type = I
NET w3[2] LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1, Type :
NET w3[3] LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type = I/O
```

David DeGraw
Lab #9: Stopwatch
3/17/2015

Anomalies:

I was sending set (start) and reset into my srLatch (probably because of the name: set and reset latch) but I really needed to send my start and stop signals. Just a little confusing.

The instructions for this lab probably should be re written as they were very hard to follow.

The flip flop in the preparation section was totally unrelated to the lab?