

David DeGraw

Lab 5 ALU

2/12/2015

## Full Adder

```
module fullAdder(s, cout, a, b, cin);
    output s, cout;
    input a, b, cin;
    wire a1, a2, a3;


    xor(s, a, b, cin);


    and(a1, a, b);
    and(a2, a, cin);
    and(a3, b, cin);
    or(cout, a1, a2, a3);
endmodule
```


```
#add all signals to the waveform viewer
wave add / -radix hex
```

```
#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns"
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat
isim force add a 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add b 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add cin 0 -time 0 -value 1 -time 40ns -repeat 80ns
```
 
```
#Nothing will change in the waveform viewer until you run the simulation for some
run 80ns
```



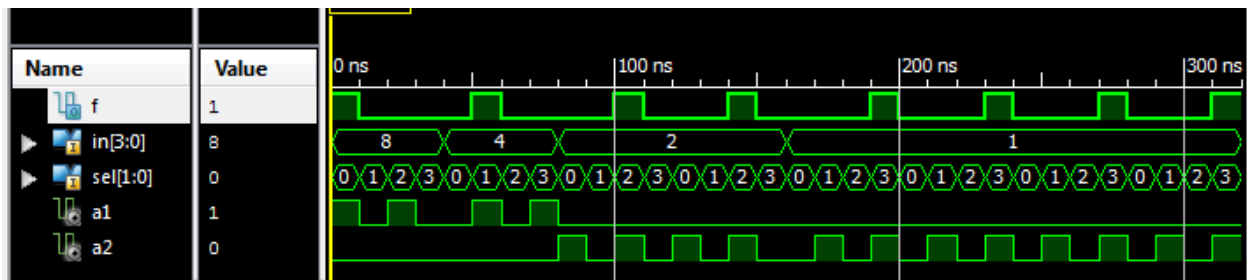

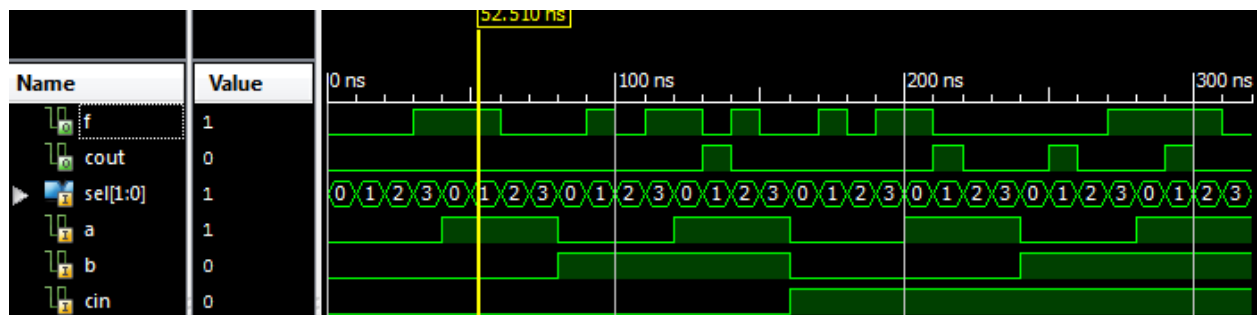

David DeGraw

Lab 5 ALU

2/12/2015

## 4 Bit ALU


```
module ALU4bit(f, cout, sel, a, b, cin);
    output [3:0] f;
    output cout;
    input [1:0] sel;
    input [3:0] a, b;
    input cin;
    wire s1, s2, s3, c1, c2, c3;

    ALU1bit a1(f[0], c1, sel, a[0], b[0], cin);
    ALU1bit a2(f[1], c2, sel, a[1], b[1], c1);
    ALU1bit a3(f[2], c3, sel, a[2], b[2], c2);
    ALU1bit a4(f[3], cout, sel, a[3], b[3], c3);
endmodule
```

```
#add all signals to the waveform viewer
wave add / -radix hex
```

```
#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns"
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat
isim force add sel 00 -time 0 -value 01 -time 10ns -value 10 -time 20ns -value 11
isim force add a 0101
isim force add b 0011
isim force add cin 0
```
 
```
#Nothing will change in the waveform viewer until you run the simulation for some
run 40ns
```



David DeGraw

Lab 5 ALU

2/12/2015

```
## Leds
NET "f[0]" LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7, Type = RHCL
NET "f[1]" LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6, Type = RHCL
NET "f[2]" LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2, Type = RHCL
NET "f[3]" LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/TRDY1, Type
#NET "Led<4>" LOC = "E17"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD
#NET "Led<5>" LOC = "P15"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD
#NET "Fan" LOC = "F4"; # Bank = 3, Pin name = IO, Type = I/O, Sch name = LD6
NET "cout" LOC = "R4"; # Bank = 3, Pin name = IO/VREF_3, Type = VREF, Sch name

## Switches
NET "b[0]" LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0
NET "b[1]" LOC = "H18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name
NET "b[2]" LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2
NET "b[3]" LOC = "K17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3
NET "a[0]" LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4
NET "a[1]" LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5
NET "a[2]" LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6
NET "a[3]" LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7

## Buttons
#NET "btn<0>" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = B
#NET "btn<1>" LOC = "D18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch na
NET "sel<0>" LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BT
NET "sel<1>" LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BT
```

## Anomalies:

I had a strange error in my 4 bit ALU, but trying to simulate my full adder would fail. I just bagged the whole thing and started a new project from scratch and re-wrote it, and it worked the second time.