

David DeGraw

3/31/2015

Lab 11 – Response Game Integration

Control FSM:

```
module stateMachine(clk, reset, stop, start, cntdone, SCupdate, msrollover, msreset, state);
    input clk, reset, msrollover, start, stop, cntdone;
    output msreset;
    output SCupdate;

    output reg [3:0] state;

    parameter s0 = 4'b001;
    parameter s1 = 4'b010;
    parameter s2 = 4'b100;

    always @ (posedge clk)
    begin
        if (reset)
            state <= s0;
        else
            case (state)

                s0 : if (start)
                    state <= s1;

                s1 : if (cntdone)
                    state <= s2;

                s2 : if (stop | msrollover)
                    state <= s0;

            endcase
        end

        assign update = (state == s2 & stop) ? 1'b1 : 1'b0;

        assign led = (state == s2) ? 1'b1 : 1'b0;

        assign msreset = (state == s1) ? 1'b1 : 1'b0;

        assign cntstart = (state == s0 & start) ? 1'b1 : 1'b0;

    endmodule
```

```
wave add / -radix hex
```


```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add start 1
isim force add reset 1 -time 0 -value 0 -time 20ns
isim force add cntdone 1
isim force add stop 1 -time 0 -value 0 -time 70ns
isim force add msrollover 0 -time 0 -value 1 -time 70ns

run 200ns
```

David DeGraw

3/31/2015

Lab 11 – Response Game Integration

 


Synchronizer:

```
module syncro(out, in, clk, clr, en);  
    input in, clk, clr, en;  
    output out;  
  
    wire w1;  
  
    FF_DCE ff1(w1, clk, in, clr, en);  
    FF_DCE ff2(out, clk, w1, clr, en);  
  
endmodule
```

```
wave add / -radix hex
```
 
```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns  
isim force add clr 1 -time 0 -value 0 -time 20ns  
isim force add en 1  
isim force add in 0 -time 0 -value 1 -time 105ns -repeat 25ns  
  
run 400ns
```



MS Counter:

```

module mscounter(rollover, sum, i, r, clk);
    output rollover;
    output [15:0] sum;
    input i, r, clk;

    wire w1, w2, w3;
    wire [3:0] s0, s1, s2, s3;

    mod10counter m1(s0, w1, i, clk, r);
    mod10counter m2(s1, w2, w1, clk, r);
    mod10counter m3(s2, w3, w2, clk, r);
    mod10counter m4(s3, rollover, w3, clk, r);


    assign sum = {s3, s2, s1, s0};

endmodule

wave add / -radix hex

isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add r 1 -time 0 -value 0 -time 20ns
isim force add i 1

run 200000ns
  
```

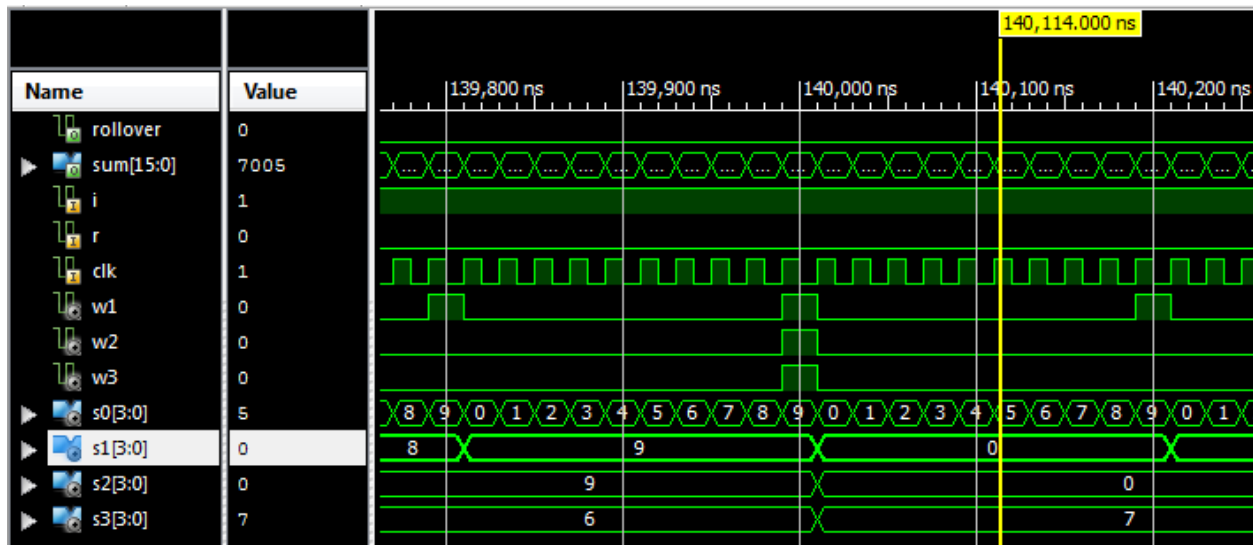

David DeGraw

3/31/2015

Lab 11 – Response Game Integration

```
wave add / -radix hex
```

```
isim force add clk 0 -time 0 -value 1 -time 10ns -repeat 20ns  
isim force add clr 1 -time 0 -value 0 -time 20ns  
isim force add startin 1  
isim force add stopin 0 - time 50ns -value 1 -time 100ns  
isim force add bestin 1  
isim force add dp 1111  
  
run 200000ns
```

Anomalies:

The bit widths on the pdf instructions were wrong. It would say like [16:0] (for a 16 bit number), but it should say [15:0].